

**ELECTRONICS & INSTRUMENTATION***Time: Three Hours**Maximum Marks: 100*

*Answer five questions, taking ANY TWO from Group A, any two from Group B and all from Group C.*

*All parts of a question (a, b, etc. ) should be answered at one place.*

*Answer should be brief and to-the-point and be supplemented with neat sketches.*

*Unnecessary long answer may result in loss of marks.*

*Any missing or wrong data may be assumed suitably giving proper justification.*

*Figures on the right-hand side margin indicate full marks.*

**Group A**

1. (a) Explain the difference in conduction among insulators, semiconductors and conductors, showing the energy band diagrams. 6
- (b) Make a comparative study between an avalanche p - n junction diode and a Zener diode. 6
- (c) State the important features of the CB, CE and CC modes of operation of a transistor. 8
2. (a) Explain active region, saturation region and cut-off region of transistor operation 6
- (b) With an appropriate circuit diagram for CE mode operation, explain fixed bias and emitter bias of transistor. With a suitable circuit parameters, find the expressions for stability of collector current with respect to  $I_{CO}$  (reverse saturation current),  $V_{BE}$  (base-emitter voltage), and beta. 8
- (c) Make a comparative study between a “Bipolar Junction Transistor (BJT)” and a “Junction Field Effect Transistor(JFET) or FET”. 6
3. (a) Draw a schematic of the physical structure of an n-channel JFET. Explain the current conduction mechanism and I-V characteristics of n-channel JFET. 6

- (b) Draw the circuit of a CE amplifier. Also, draw its small signal equivalent circuit. Derive expressions for input impedance, output impedance, voltage gain, and current gain. 8
- (c) Discuss in detail the reasons (advantages) for opting negative feedback in transistor amplifiers. 6
4. (a) What are the differences between a transistor and a thyristor? Discuss operation of a thyristor with help of its characteristics. Also, mention at least three applications of thyristors. 6
- (b) How op-amp can be used as a (i) Summer (ii) Differentiator (iii) Integrator? Derive the output voltage equation for both the cases. 6
- (c) With a neat schematic, explain the operation of a 'successive approximation register' type analog to digital converter circuit using op-amp. Mention its advantages and disadvantages with respect to other methods of A/D converters. 8

**Group B**

5. (a) Describe, with a neat sketch, the constructional feature and working principle of a dynamometer type wattmeter. Deduce the expression for torque produced. 10
- (b) Draw a neat diagram of a permanent magnet moving coil instrument and explain its working. 10
6. (a) Explain the operation of PMMC-type voltmeter. Establish the working formula. A moving coil instrument has the following data: Number of turns = 100, width of coil = 20 mm, depth of coil = 30 mm, flux density in the gap =  $0.1 \text{ Wb/m}^2$ . Calculate the deflecting torque when carrying a current of 10 mA. Also, calculate the deflection, if the control string constant is  $2 \times 10^{-6} \text{ Nm/degree}$ . Ignore friction involved. 10
- (b) With a neat schematic, explain the operation of a Q- meter. 10
7. (a) What are the differences in the following electronic voltmeters: (i) peak reading type, (ii) rms reading type, and (iii) average reading type. Explain briefly using schematic diagrams. 10

- (b) Write short notes on any two of the following : (i) Spectrum analyzer (ii) RF signal generator (iii) Distortion meters. 10
8. (a) What is a strain gauge? With a neat schematic diagram, explain its operation. Prove that for a strain gauge, the gauge factor is given by  $K = 1 + 2\mu$  where  $\mu$  is the Poisson's ratio. 10
- (b) With a neat schematic, explain how the level of water in a tank of a multistoried building can measure without moving at the roof top. 10

**Group C**

9. Select the right choice. 20
- (i) The controlling torque in a spring controlled indicating instrument is proportional to
- (a)  $\theta$
  - (b)  $\theta^2$
  - (c)  $1/\theta$
  - (d)  $1/\theta^2$
- (ii) In the measurement of three-phase power by two wattmeter method, if two wattmeter readings are equal, the power factor of the circuit is
- (a) 0
  - (b) 0.8 lagging
  - (c) 0.8 leading
  - (d) unity.
- (iii) Which of the following meter is integrating type ?
- (a) Moving iron voltmeter
  - (b) Rectifier type ammeter
  - (c) Induction type energy meter .
  - (d) Dynamometer type wattmeter.
- (iv) The principle of operation of LVDT is based on variation of
- (a) self-inductance
  - (b) mutual inductance
  - (c) reluctance

- (d) performance.
- (v) Transistor, as a digital device, operates in
- (a) active region only
  - (b) cut-off condition only
  - (c) salutation condition only
  - (d) bath cutoff and saturation conditions
- (vi) The common emitter amplifier provides phase shift of
- (a)  $360^\circ$
  - (b)  $270^\circ$
  - (c)  $180^\circ$
  - (d)  $90^\circ$
- (vii) A transistor is operating in active region. Under this condition,
- (a) both the junctions are forward biased
  - (b) both the junctions are reverse biased
  - (c) emitter-base junction is reverse biased, collector-base junction is forward biased
  - (d) emitter-base junction is forward biased, collector-base junction is reverse biased.
- (viii) In a p-n junction biased in the forward direction, the holes
- (a) cross the junction from n-type into p-type region
  - (b) remain stationary in the p-type region
  - (c) cross the junction from p-type into n type region
  - (d) remain stationary in the n-type region.
- (ix) The amplifier is said to have negative feedback when:
- (a) any decrease in the output signal results in a feedback signal into (he input in such a way as to cause a decrease in the output signal
  - (b) any decrease in the input signal results in a feedback signal into the output in such a way as to cause an increase in the output signal
  - (c) any increase in the input signal results in a feedback signal into the input in such a way as to cause a decrease in the output signal
  - (d) any increase in the output signal results in a feedback signal into the input in such a way as to cause a decrease in the output signal.
- (x) The p-channel MOSFET consists of

- (a) a lightly doped n-type substrate into which two highly doped  $p^+$  regions are diffused
- (b) a lightly doped n type substrate into which two highly doped  $n^+$  regions are diffused
- (c) a highly doped n-type substrate into which one highly doped  $p^+$  region is diffused
- (d) a highly doped p-type substrate into which two highly doped  $p^+$  regions are diffused.

*(Refer our course material for answers)*