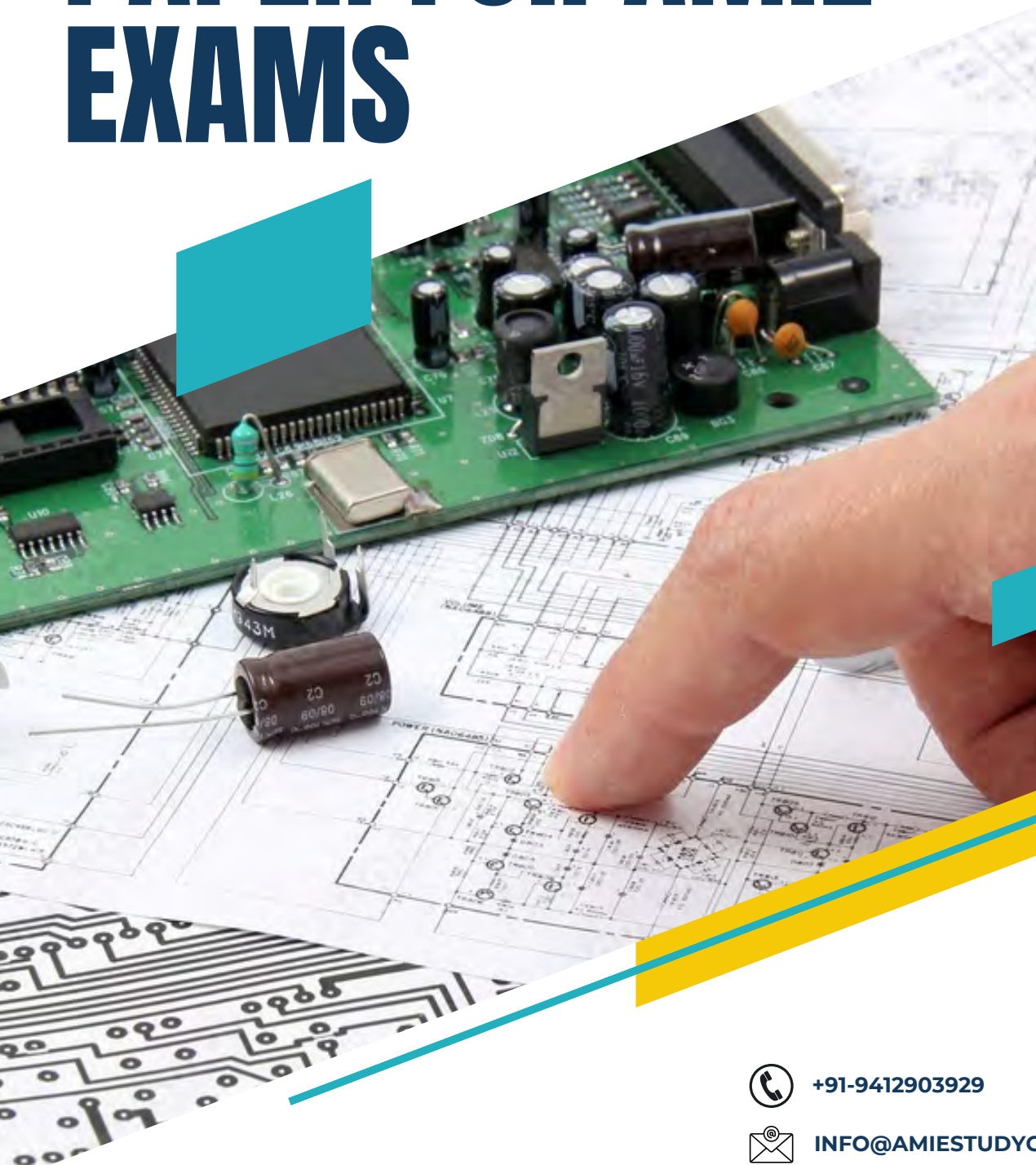


# MODEL TEST PAPER FOR AMIE EXAMS



## DESIGN OF ELECTRONIC DEVICES & CIRCUITS

TEST PAPER 1



+91-9412903929



INFO@AMiestudycircle.com



CITY PRIDE COMPLEX, NR IIT CAMPUS,  
ROORKEE



AMiestudycircle.com

**DESIGN OF ELECTRONIC DEVICES & CIRCUITS**

*Time: Three Hours*

*Maximum Marks: 100*

*Answer five questions, taking ANY TWO from Group A, any two from Group B and all from Group C.*

*All parts of a question (a, b, etc. ) should be answered at one place.*

*Answer should be brief and to-the-point and be supplemented with neat sketches.*

*Unnecessary long answer may result in loss of marks.*

*Any missing or wrong data may be assumed suitably giving proper justification.*

*Figures on the right-hand side margin indicate full marks.*

**Group A**

1. (a) What is an integrated circuit? How does it differ from a discrete circuit? 6  
Discuss the relative merits and demerits of ICs over discrete circuits.
- (b) Draw the functional block diagram of an op-amp and explain the operation 6  
of each block. Also write down the characteristics of an ideal op-amp.
- (c) Explain the following terms in connection with operational amplifiers: 8
  - (i) Common mode rejection ratio
  - (ii) Virtual ground
  - (iii) Inverting and non inverting modes of operation
  - (iv) Input and output offset voltage
  
2. (a) Difference mode gain of a diff amplifier is 2000. Calculate the output 8  
voltages for (i) CMRR = 100 and (ii) CMRR = 10,000; if the inputs are  $V_1 = 1.0$  mV and  $V_2 = 0.9$  mV and show the effect of high CMRR. Assume  $V_i$  applied of 1 mV input.
- (b) Using a neat sketch, explain the working of a sample and hold circuit. What 6  
are the applications of sample and hold circuits. How can the hold time be controlled?
- (c) Explain some of the linear and non linear applications of OPAMP by giving 6  
suitable examples.

3. (a) Design a second order low pass Butterworth filter with a cut-off frequency of 1 kHz and a pass band gain of 3. Use a capacitor of value 0.01  $\mu$ F. Also plot its gain frequency response. 8
- (b) What does an unregulated power supply consist of? State three disadvantages of an unregulated power supply. 6
- (c) Draw the circuit diagram of a simple Zener diode voltage regulator and explain how the circuit operates. 6
4. (a) Draw the circuit and explain the working of a series pass transistor voltage regulators. make a comparison between a series and shunt voltage regulator. 6
- (b) Distinguish between positive and negative voltage regulators. Write down the advantages and disadvantages of positive and negative voltage regulators. 6
- (c) Explain "fold back current limiting" technique. How does it eliminate the limitation of constant current limiting circuit. Describe its output characteristics. 8

**Group B**

5. (a) Write down the condition for oscillation in an oscillator circuit. How oscillation builds up in any oscillator circuit? 4
- (b) With a neat schematic explain the operation of an RC phase shift oscillator. Also derive expressions for its frequency of operation and condition for sustaining oscillation. 8
- (c) Sketch the circuit of a Wien bridge oscillator. Find an expression for frequency of oscillations in Wein bridge oscillator. Show that amplifier used in a Wein bridge oscillator must have a gain greater than 3 for sustained oscillations. 8
6. (a) Derive the expression for  $f_s$  and  $f_p$  of crystal oscillator. Also sketch its equivalent circuit. Write down some advantages and disadvantages of a crystal oscillator. 6
- (b) Design an stable multivibrator which has a frequency of oscillation of 10 kHz and duty cycle of 75%. derive the necessary mathematical steps for the design. 8

Hint: Take astable multivibrator. You may assume  $R_B$  as  $10\text{ k}\Omega$  to start with.

- (c) The 555 IC timer is connected as a free running multivibrator. Determine the frequency of oscillation. Given  $R_A = R_B = 1\text{ kW}$  and  $C = 1000\text{ pF}$ . The symbols used have the usual meaning. 6
7. (a) Explain DSB-SC (double sideband suppressed carrier) modulation. Obtain the expression or single tone DSB-SC modulated wave and find its spectrum. Plot it in time-domain and frequency domain. 7
- (b) Draw and explain the block diagram of a superheterodyne receiver. 6
- (c) What is a PLL? How does it work? Discuss its applications. With the help of a block diagram and necessary equations, explain the Phase Locked Loop demodulator for a FM wave. 7
8. (a) Draw the block diagram of a ramp type digital voltmeter and explain its working. How can it be modified for multiple range of measurements? 7  
Hint: Describe ramp type A/D converter.
- (b) Explain the working of dual slope ADC. Explain how noise rejection is obtained. 6
- (c) Draw the block diagram of a frequency meter (frequency counter) and explain its working. Sketch system waveforms. 7

### *Group C*

9. Answer the following in brief: 20
- (i) The ideal Op Amp has the following characteristics
- (a)  $R_i = \infty$ ;  $A_v = \infty$ ;  $R_0 = 0$
- (b)  $R_i = 0$ ;  $A_v = \infty$ ;  $R_0 = 0$
- (c)  $R_i = 0$ ;  $A_v = 0$ ;  $R_0 = 0$
- (d)  $R_i = \infty$ ;  $A_v = \infty$ ;  $R_0 = \infty$
- (ii) Which type of Analog to Digital Converter is the fastest
- (a) Successive approximation register
- (b) Dual slope ADC
- (c) Flash ADC

- (d) Pipelined ADC
- (iii) An ideal Op-Amp is a
- (a) Voltage-controlled current source
  - (b) Voltage-controlled voltage source
  - (c) Current controlled current source
  - (d) Current-controlled voltage source
- (iv) From the power saving option which modulation technique is preferred
- (a) AM
  - (b) DSBSC
  - (c) VSB
  - (d) FM
- (v) A non-inverting amplifier with a gain of 100 is nulled at 25°C. Determine the output voltage if the temperature rises to 40°C for an offset voltage drift of 0.15 MV/°C.
- (a) 600 MV
  - (b) 450 MV
  - (c) 225 MV
  - (d) 60 MV
- (vi) A second-order low-pass filter has a roll-off rate of
- (a) - 40 dB/octave
  - (b) - 40 dB/decade
  - (c) - 20 dB/octave
  - (d) - 20 dB/decade
- (vii) A PLL that is very useful as an FSK. demodulator is
- (a) 565 PLL
  - (b) 564 PLL
  - (c) 562 PLL
  - (d) 561 PLL
- (viii) Consider a 1024-bit ROM. How many address bits does it require?
- (a) 16
  - (b) 12
  - (c) 10

- (d) 8
- (ix) An astable multivibrator also known as
- (a) One shot multivibrator
  - (b) Free-running multivibrator
  - (c) Bistable multivibrator
  - (d) Monostable multivibrator
- (x) In a DVM, a signal conditioning circuit is used
- (a) To bring current to a suitable limit
  - (b) To bring resistance to a suitable limit
  - (c) To bring resistance to a suitable limit
  - (d) To bring voltage to a suitable limit

*(Refer our course material for answers)*